

EE 206
Assignment


- Priyanshu Nayak
- 240102074.

Given: $V_{th} = 0.37V$, $V_{tp} = 0.39V$

$\mu_{ncox} = 230 \mu A/V^2$, $\mu_{pcox} = 100 \mu A/V^2$

$V_{dd} = 1.8V$, $\lambda_{min} = 0.18 \mu m$, $\omega_{min} = 0.27 \mu m$

Open loop circuit diagram.

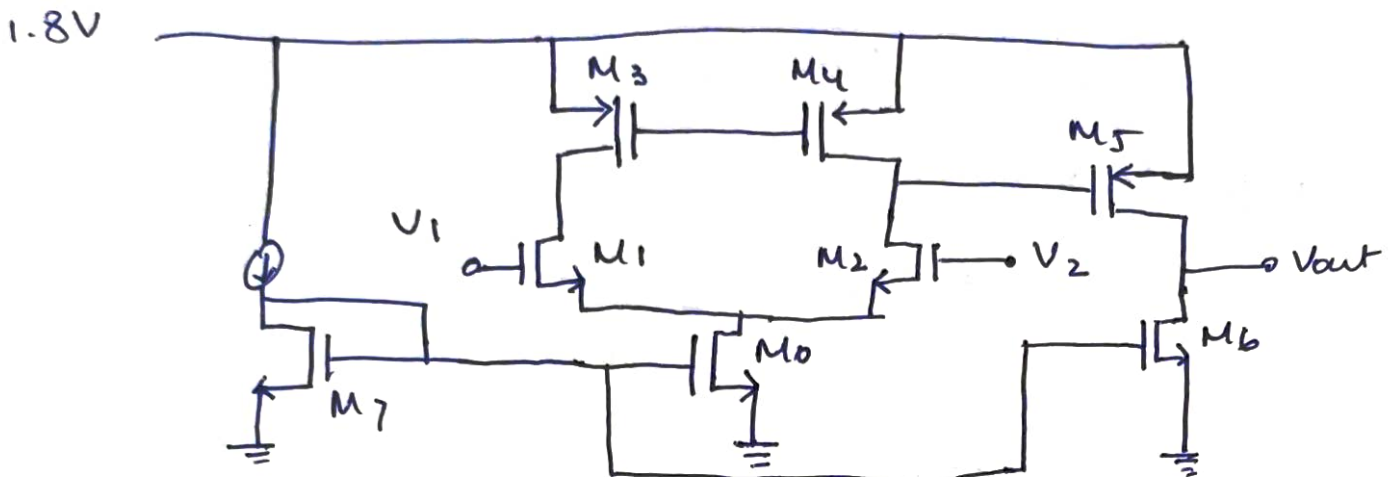

Calculations:->

$V_2 = AC$ signal of $0.1mV$ amplitude } for max swing.
 $V_1 = 0.9V_{dc}$

for M_7 transistor:

- Assuming $0.2V$ overdrive, we get :->

I_{ref} chosen as $5\mu A$:

$$\Rightarrow I_{ref} = \frac{\mu_{ncox}}{2} \left(\frac{\omega}{\lambda} \right)_7 (V_{gs} - V_{th})^2$$

Solving we get,

$$\left(\frac{\omega}{\lambda} \right)_7 = 1.09.$$

Given: $\lambda_{min} = 0.18 \mu m = 18 \times 10^{-8} = 180 nm$

$\omega_{min} = 0.27 \mu m = 270 nm$

$$\therefore \lambda = 400 nm \text{ (lets take)}$$

$$\omega = \underline{98.1 nm}$$

• for M_0 : $\rightarrow$

$$\Rightarrow I_0 = 10 I_{ref} = 50 \mu A$$

As overdrive and $\mu_n C_{ox}$ are same

$$\Rightarrow \frac{(W/L)_0}{(W/L)_7} = 10$$

$$\therefore \left(\frac{W}{L}\right)_0 = 10 \cdot 9$$

$$\begin{aligned} \text{So, } L &= 900 \text{ nm} \\ W &= 9810 \text{ nm} \\ &= 9.81 \mu m \end{aligned}$$

$$\text{Also, } V_s > (V_{gs} - V_{th})$$

$$\Rightarrow \boxed{V_s > 0.2 \text{ V}}$$

• for M_1 and M_2 transistor : $\rightarrow$

$$I_1 \text{ and } I_2 = \frac{50}{2} \mu A = 25 \mu A$$

choosing the overdrive 0.2 V.

$$\frac{(W/L)_1}{(W/L)_0} = \frac{1}{2}$$

$$(\text{as } I_1 = I_2 = I_0/2)$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = \frac{1}{2} \times 10 \cdot 8 = 5.45$$

$$\text{So, as } L_1 = L_2 = 900 \text{ nm.}$$

$$W_1 = W_2 = 4.91 \mu m.$$

Now,

$$V_{gs} - V_{th} = 0.2 \text{ V}$$

$$\Rightarrow 0.9 \text{ V} - V_s - 0.37 \text{ V} = 0.2 \text{ V}$$

$$\Rightarrow V_s = (0.9 - 0.37 - 0.2) \text{ V}$$

$$\therefore V_s = 0.33 \text{ V} > 0.2 \text{ V} \text{ so, } M_0 \text{ is in saturation.}$$

$$\text{Now, } V_{D1} > (V_{gs} - V_{th})_1$$

$$\underline{\underline{V_{D1} > 0.2 \text{ V}}}$$

$\Rightarrow$ for M_3, M_4

$$I_3 = I_4 = 25 \mu A.$$

$$I_3 = \frac{1}{2} \mu_p C_{ox} (V_{gs1} - V_{th1})_3^2 \left(\frac{W}{L}\right)_3$$

$$\Rightarrow \frac{25}{50} = \left(\frac{W}{L}\right)_3 (V_{gs1} - V_{th1})_3^2$$

Taking $\left(\frac{W}{L}\right)_3 = 10$

$$(V_{GS} - V_{TH})_3 = 0.223V$$

So, $(V_{GS} - V_{TH})_4 = 0.223V$

and $\omega_3 = \omega_4 = 9\mu m$

$L_3 = L_4 = 900nm$

Now, for M_3 to be ON,

$$V_{GS} > |V_{TP}|$$

$$\Rightarrow V_{GS} > |V_{TP}|$$

$$\Rightarrow 1.5V - |V_{TP}| > V_G$$

$$\Rightarrow V_G < (1.8 - 0.39)V$$

$$\therefore V_G < \underline{1.41V}$$

We get, $(V_{GS} - V_{TH})_3 = 0.223V$

$$\Rightarrow 1.8V = 0.223 + V_{D1} + 0.33$$

$$\underline{V_{D1} = 1.189V}$$

Clearly it satisfies $V_{D1} > 0.2V$ and $V_{D1} < 1.41V$

So M_3 and M_4 } Are in
 M_1 and M_2 } saturation.

$\therefore$ Gain due to first stage $= g_{m2} (r_{on2} || r_{op4})$

(taken from logfile) $= -102.06$

practically $= -23.02$

$\therefore$ $\underline{A_{vol} = 187}$

practically, $V_{D1} = V_{mid} \approx 1.102V$ (as V_{in} varies due to body effect)

* M_6 : $I_b = 25\mu A$ as

$V_{G7} = V_{G6}$

$$\Rightarrow 25\mu A = \frac{1}{2} (230A \times \left(\frac{\omega}{L}\right)_6 \times (0.2)^2$$

$$\Rightarrow \left(\frac{\omega}{L}\right)_6 = \frac{25 \times 2}{230 \times 0.2^2}$$

$$\therefore \left(\frac{W}{L}\right)_6 = 5.435$$

$$\therefore L_6 = 900 \text{ nm}$$

$$W_6 = 4.892 \mu\text{m}$$

Practically $W_6 = 4.628 \mu\text{m}$

$$L_6 = 900 \text{ nm}$$

$$I_6 = 29.3 \mu\text{A}$$

$$\begin{aligned} * M_5: (V_{GS} - V_{TH})_5 &= V_5 - V_{M1} - V_{TH} \\ &= 1.8 - 1.187 - 0.39 \\ &= \underline{\underline{0.223 \text{ V}}} \end{aligned}$$

$$I_5 = 25 \mu\text{A}$$

$$\Rightarrow \left(\frac{W}{L}\right)_5 = \frac{25 \times 2}{100 \times (0.223)^2} = 10$$

$$L_5 = 900 \text{ nm}$$

$$W_5 = 9 \mu\text{m}$$

$$\begin{aligned} \text{So gain of second stage} &= g_{m5} \times (r_{op5} \parallel r_{on6}) \\ &= -9.14 \times 10^{-5} \times (279329.608) \\ &= \underline{\underline{-25.530}} \end{aligned}$$

$$\therefore \text{Theoretical gain} = 2605.59$$


$$\& \text{ practically, open loop gain of OTA} \Rightarrow \underline{\underline{3027.82}}$$

$$\text{first stage as } \underline{\underline{83.02}}$$

$$\text{second stage as } \underline{\underline{36.47}}$$

$$\therefore \text{error} \approx 16\%$$

Closed loop $\Rightarrow$

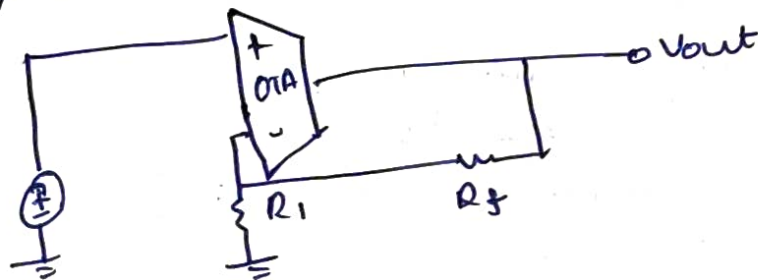

$$V_{out} = (V_+ - V_-)A$$

$$\Rightarrow V_- = V_{in} - \frac{V_{out}}{A} = \frac{(AV_{in} - V_{out})}{A}$$

$$\text{So KCL: } \frac{\frac{AV_{in} - V_{out}}{A}}{R_1} + \frac{(AV_{in} - V_{out})}{A} - V_{out} = 0$$

$$\Rightarrow V_{in} \left[\frac{R_1 + R_f}{R_1 R_f} \right] = V_{out} \left(\frac{R_f + AR_1 + R_1}{R_1 R_f} \right)$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A(R_1 + R_f)}{(1+A)R_1 + R_f}$$

$$= \left(1 + \frac{R_f}{R_1} \right) \left(\frac{A}{(1+A) + \frac{R_f}{R_1}} \right)$$

$$\text{So choosing } R_f = 21 \text{ k}\Omega$$

$$R_1 = 20 \text{ k}\Omega$$

$$A = 23$$

$$\frac{V_{out}}{V_{in}} = \left(1 + \frac{21}{20} \right) \left(\frac{3027.82}{3027.82 + \frac{21}{20}} \right)$$

$$\therefore \frac{V_{out}}{V_{in}} \approx 2.049$$

Also practically getting

$$\frac{V_{out}}{V_{in}} \approx 2.035$$

$$\therefore \text{error} = -0.64\%$$

$$\begin{cases} C_f = 10 \text{ pF} \\ C_c = 3 \text{ pF} \end{cases}$$

$$\text{Power distribution} =$$

$$(5 + 50 + 45) \times 1.8$$

$$= 1.44 \times 10^{-4} \text{ W}$$

$$= \underline{\underline{0.144 \text{ mW}}}$$